

Physics

Important Numericals


- ① A Diverging Lens of focal length 15 cm form an image 10 cm from lens. Calculate the distance of object from lens. (Ans \rightarrow 30 cm)
- ② A thin prism of angle 5° angle gives minimum deviation of 3.2° . Calculate the refractive index of prism. (Ans \rightarrow 1.14)
- ③ A house wiring supplied with 220 volt supply protected by 6A fuse. Calculate the maximum number of 60 Watt bulb in parallel that can be flow. (Ans - 2)
- ④ 4.5 cm needle is placed 12 cm away from a Convex Mirror of focal length 5 cm find the position, size and nature of image. (Ans - 1.7, / 3.6, Virtual)
- ⑤ A needle of 3 cm size placed 25 cm away from a Concave mirror of focal length 10 cm. find position, size and nature of image. (Ans - 11.67 cm, 2 cm, Real)
- ⑥ A resistance of a wire is 2Ω . Calculate its new Resistance if
(a) length of wire become 2 times (b) length 2 times by stretching
(c) wire become doubled up by folding (d) diameter become half
(e) diameter become 2 times. (Ans - (a) 4Ω (b) 8Ω (c) 5Ω (d) 8Ω (e) 5Ω)
- ⑦ An electric heating element consume 500 Watt when Voltage is 100 volt. If Voltage become 150 volt Calculate the power consumed. (Ans 1125 W)
- ⑧ Two lens first is Convex of focal length 20 cm and second is Concave of focal length 6 cm . find the total length, Power and nature of combination. (30 cm, 3.30)
- ⑨ Two Thin lenses are placed in contact and focal length of the combination is 8 cm . If focal length of one lens is 20 cm . find the focal length and power of other lens. (Ans - 16 cm, -3.75 D)
- ⑩ Three resistance 1Ω , 2Ω and 3Ω are Connected in series by supply of 12 Volt. find Potential difference at each Resistance. (Ans - 2V, 4V, 6V)
- ⑪ Three Resistance 1Ω , 2Ω and 3Ω are Connected in parallel by a battery of 10 Volt Calculate (i) Total Resistance (ii) Voltage on each resistance. (iii) Current on each Resistance. (Ans - 5Ω , 10 Volt, 1A, 0.5A, 0.33A)
- ⑫ A ray of light falling at angle of 45° is reflected through a prism and suffer minimum deviation prism angle is 6° . find the refractive index for prism. (Ans $\sqrt{2}$)

- (13) A ray falls on Equilateral prism and suffer minimum deviation of 6° . find the refractive index for prism. (Ans - 1.5)
- (14) Calculate the heat produced by 200W heater in 5 minute. (Ans - 6000 J)
- (15) If a bulb of 100Watt is connected by 200 volt supply. find Resistance and Current. (Ans - 400 Ω , 0.5A)
- (16) A Concave Lens of focal length 15cm form an image 10cm from the lens. How far object placed also find magnification. Draw - ray diagram. (Ans - 30cm, $m = 0.5$)
- (17) Three Resistance are connected in parallel draw current 7.5A by 30 volt battery. Two resistance have 1Ω and 12Ω . find out third resistance and current through each resistance. (Ans - 15Ω , 3A, 2.5A, 2A)
- (18) A current 5mA passes through Resistance of 2200Ω and Voltage. (Ans - 11V, 11V)
- (19) find speed of light in glass if its refractive index is $\frac{3}{2}$. (Ans - 2×10^8 m/s)
- (20) An object ht 6cm is placed at a distance of 10cm from a Convex Mirror with radius of curvature 30cm. find position size and nature of image. (Ans - 15cm, 2cm, virtual)
- (21) Two lenses of 100W and 60W are connected in parallel by supply of 220 Volt. Calculate Current drawn. (Ans - 0.75A)
- (22) Two lenses of focal length 20cm and 30cm are placed in contact find the focal length and power of combination. (Ans - 12cm, 8.33D)
- (23) Two lens of power 3.5D and -1.5D are placed in contact find focal length and power of combination. (Ans - 20, 50cm)
- (24) find the Critical Angle of a medium whose refractive index is $\frac{4}{3}$. (Ans - 61°)
- (25) Three Resistance of 2Ω , 4Ω and 6Ω are connected in series by supply of 12 Volt. Calculate (i) Total Resistance (ii) Current on each resistance (Ans - 1A, 2V, 4V, 6V)


(26) find Equivalent Resistance b/w A and B



Ans - $\frac{11}{3}\Omega$

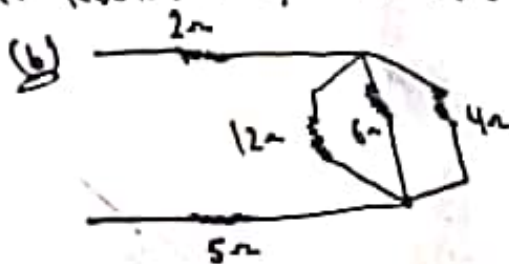

Ans - 2Ω

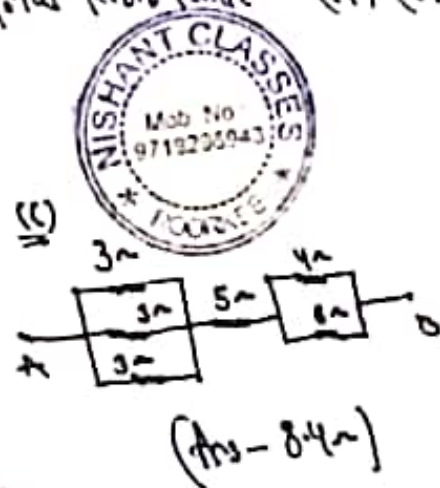

- (27) A wire of uniform thickness with a resistance of 27Ω is cut into three equal pieces and they are joined in parallel. find the resistance in parallel combination. (Ans - 3Ω)
- (28) What current will be required by a lamp marked 225 V and 40 W ? find resistance of this lamp and heat produced in 5 minutes (Ans - 0.18 A , 1265.6 J)
- (29) There are three Resistance 10Ω , 15Ω and 30Ω . find the ratio in the minimum and Maximum Resistance in this combination (Ans - $4:39$)
- (30) A ray falls on a prism and suffer minimum deviation at 40° . if prism angle is 60° . find refractive index for prism. (Sin $50^\circ = 0.7660$) (Ans - 1.524)
- (31) for a thin prism, its angle of minimum deviation is 5° and prism angle is 6° find refractive index for prism (Ans - 1.83)
- (32) An object 5 cm size is placed at the focus of convex lens of focal length 10 cm . find position size and nature of image. Draw Ray diagram also. (-5 cm , 2.5 cm , Virtual)
- (33) If two bulbs of 25 Watt and 100 W each rated 220 V are connected in series with supply of 440 V . Then calculate potential across both the bulbs. Comment whether any bulb will fuse? (352 V , 88 V)
- (34) A wire of Resistance 25Ω is drawn out into thin wire due to this its length become 3 times. find new Resistance. (Ans - 9Ω)
- (35) find Equivalent Resistance b/w A and B
- (36) A needle of size 4.5 cm is placed at distance of 12 cm from a convex mirror of focal length 15 cm . find position, size and nature of image. (Ans - 6 cm , 2.5 cm , Virtual, Erect)
- (37) Two lens of power $+3.5\text{ D}$ and -4.75 D are placed in contact. find the focal length of combination (Ans - 2 m)
- (38) Two lenses of focal length 20 cm and 50 cm are placed on same axis at 20 cm . find equivalent focal length and power (Ans - 20 cm , 5 D)
- (39) There is a prism of angle 60° has refractive index $\sqrt{2}$. In case of minimum deviation find its angle of deviation (Ans - 30°)



In a coil the value of Magnetic flux decreases from 12×10^{-3} Weber to 6×10^{-3} wb in 0.1 sec. Calculate EMF induced in coil (Ans - 0.6 volt)

(41) An electron enters in Magnetic field at 5×10^7 m/sec at angle 30° . If Magnetic field is 1 Tels. find Magnetic force on it. (Ans - 4×10^{-12} Newton)

(42) There is a straight wire of length 10 cm having 10 Ampere in it. placed perpendicularly in magnetic field of 5 Tels. find Magnetic force on it (Ans - 5 Newton)

(43) The current of 10 Ampere flows in a straight wire. find Magnetic field at a point 10 cm away from it (Ans - 2×10^{-5} Tels)

(44) The current of 10 A flows in a circular wire of radius 10 cm. find Magnetic field at its centre. It has 100 turns. (Ans - 2×10^{-2} Tels)

(45) The far point of a myopic person is 80 cm. What is the nature and power of lens required to correct defect. (Ans - -1.25 D, Concave lens)

(46) The near point of hypermetropic eye is 1 m. find the nature and power of lens required to correct defect (Ans - 3 D, Convex lens)

(47) An electric oven of 2 kW power rating is operated in a domestic electric circuit (220 V) that has a current rating of 5 A. What would you expect? (fuse blows)

(48) A circuit has a fuse of 5 A. What is the maximum number of 100 W (220 V) bulbs that can be safely used in the circuit? [x = 11]

(49) What is the maximum number of 60 W bulbs that can be run from the main supply of 220 volts if you do not want to overload a 5 A fuse? [18 bulbs]

(50) A 1.25 kW heater works on a 220 V mains supply. What current rating would a suitable fuse have? [10 A]



Q51 An electric lamp of $100\ \Omega$, a toaster of resistance $50\ \Omega$, and a water filter of resistance $500\ \Omega$ are connected in parallel to a 220 V source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it? (7.04 A)

Q52 How can three resistors of resistance $2\ \Omega$, $3\ \Omega$ and $6\ \Omega$ be connected to give a total resistance of (a) $4\ \Omega$, (b) $1\ \Omega$? ($2\ \Omega$, $4\ \Omega$ and $1\ \Omega$)

Q53 What is (a) the highest, and (b) the lowest, total resistance that can be secured by the combination of four coils of resistance $4\ \Omega$, $8\ \Omega$, $12\ \Omega$, $124\ \Omega$? ($48\ \Omega$, $2\ \Omega$)

Q54 Compute the heat generated while transferring 96000 coulombs of charge in one hour through a potential difference of 50 V . ($4.8 \times 10^6\text{ J}$)

Q55 An electric iron of resistance $20\ \Omega$ takes a current of 5 A . Calculate the total heat developed in 30 s . (15000 J)

Q56 An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h . ($7.92 \times 10^6\text{ J}$)

Q57 An electric bulb is rated 220 V and 100 W . When it is operated on 110 V , the power consumed calculate. (25 W)

Q58 When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor. ($4800\ \Omega$)

Q59 A battery of 9 V is connected in series with resistors of $0.2\ \Omega$, $0.3\ \Omega$, $0.4\ \Omega$, $0.5\ \Omega$ and $12\ \Omega$ respectively. How much current would flow through the $12\ \Omega$ resistor? ($I = 0.67\text{ A}$)

Q60 How many $176\ \Omega$ resistors in parallel are required to carry 5 A on a 220 V line. ($n = 4$)

Q61 Several electric bulbs designed to be used on a 220 V electric supply line are rated 10 W each. How many bulbs can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A ? (110 bulbs)



Two lamps, one rated 100W at 220V and the other 60W at 220V are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220V?
($I = 0.727A$ or $0.73A$)

Q₆ Which uses more energy, a 250W TV set in 1hr or a 1200W toaster in 10min? ($E = 0.20kWh$)

Q₇ An electric heater of resistance 8Ω draws 15A from the service mains for 2 hours. Calculate the rate at which heat is developed in the heater. ($P = 1800W$)

Q₈ Find the focal length of a convex mirror whose radius of curvature is 32cm. ($f = 16cm$)

Q₉ Find the power of a concave lens of focal length 2m. ($-0.5D$)

Q₁₀ An object 5cm in length is held 25cm away from a converging lens of focal length 10cm. Draw the ray diagram and find the position, size and nature of the image formed.
(16.67, $-3.3cm$)

Q₁₁ A concave lens of focal length 15cm forms an image 10cm from the lens. How far is the object from the lens? Draw the ray diagram. ($u = -30cm$)

Q₁₂ An object 5.0cm in length is placed at a distance of 20cm in front of a convex mirror of radius of curvature 30cm. Find the position of the image, its nature and size. (2.1cm)

Q₁₃ An object of size 7.0cm is placed at 27cm in front of a concave mirror of focal length 18cm. At what distance from the mirror should a screen be placed so that a sharp focussed image can be obtained? Find the size and nature of the image. (14.0cm)

Q₁₄ Find the focal length of a lens of power $-2.0D$. What type of lens is this? ($f = -50cm$)

Q₁₅ A doctor has prescribed a corrective lens of power $+1.5D$. Find the focal length of the lens. Is the prescribed lens diverging or converging? ($f = +66.7cm$)

Q₁₆ The filament of a lamp is 80cm from a screen and a converging lens forms an image of it on a screen, magnified three times. Find the distance of lens from the filament and the focal length of the lens. (30cm, 40cm)

